IEC TR 62001-1

Edition 2.0 2021-07

TECHNICAL REPORT

colour inside

High-voltage direct current (HVDC) systems – Guidance to the specification and design evaluation of AC filters – Part 1: Overview

INTERNATIONAL ELECTROTECHNICAL COMMISSION

ICS 29.200

ISBN 978-2-8322-9986-9

Warning! Make sure that you obtained this publication from an authorized distributor.

® Registered trademark of the International Electrotechnical Commission

CONTENTS

FOREWORD 7
INTRODUCTION 9
1 Scope 10
2 Normative references 10
3 Terms and definitions 10
4 Outline of specifications of AC filters for HVDC systems 11
4.1 General 11
4.2 Boundaries of responsibility 12
4.3 Scope of studies 14
4.4 Scope of supply 14
4.5 Technical data to be supplied by contractor 15
4.6 Alternative proposals by bidders 15
5 Permissible distortion limits 16
5.1 General 16
5.2 Voltage distortion 17
5.2.1 General 17
5.2.2 Definitions of performance criteria 17
5.2.3 Discussion and recommendations 18
5.2.4 Determination of limits 18
5.2.5 Pre-existing harmonic levels 21
5.2.6 Relaxed limits for short term and infrequent conditions 22
5.2.7 Treatment of interharmonic frequencies 22
5.3 Distortion limits pertaining to the HV and EHV network equipment 23
5.3.1 HVAC transmission system equipment 23
5.3.2 Harmonic currents in synchronous machines 23
5.3.3 Nearby HVDC installations 24
5.4 Telephone interference 24
5.4.1 General 24
5.4.2 Causes of telephone interference 24
5.4.3 Definitions of performance criteria 24
5.4.4 Discussion 25
5.4.5 Determination of limits 25
5.4.6 Pre-existing harmonic levels 27
5.4.7 Limits for temporary conditions 27
5.5 Special criteria 28
6 Harmonic generation 28
6.1 General 28
6.2 Converter harmonic generation 28
6.2.1 Idealized conditions 28
6.2.2 Realistic conditions 30
6.3 Calculation methodology 32
6.3.1 General 32
6.3.2 Harmonic currents for performance, rating and other calculations 32
6.3.3 Combining harmonics from different converter bridges 33
6.3.4 Consistent sets 33
6.3.5 Harmonic generation for different DC power ranges 34

6.4 Sensitivity of harmonic generation to various factors 35
6.4.1 Direct current, control angle and commutation overlap 35
6.4.2 Effect of asymmetries on characteristic harmonics 35
6.4.3 Converter equipment parameter tolerances 35
6.4.4 Tap steps 36
6.4.5 Theoretically cancelled harmonics 36
6.4.6 Negative and zero sequence voltages 36
6.4.7 Converter transformer saturation 37
6.4.8 Harmonic interaction across the converter 37
6.4.9 Back-to-back systems 38
6.5 Externally generated harmonics 38
7 Filter arrangements 38
7.1 Overview 38
7.2 Advantages and disadvantages of typical filters 39
7.3 Classification of filter types 40
7.4 Tuned filters 40
7.4.1 Single tuned filters 40
7.4.2 Double tuned filters 42
7.4.3 Triple tuned filters 44
7.5 Damped filters 45
7.5.1 Single tuned damped filters 45
7.5.2 Double tuned damped filters 48
7.6 Choice of filters 49
8 Filter performance calculation 50
8.1 Calculation procedure 50
8.1.1 General 50
8.1.2 Input data 50
8.1.3 Methodology 50
8.1.4 Calculation of converter harmonic currents 51
8.1.5 Selection of filter types and calculation of their impedances 52
8.1.6 Calculation of performance 52
8.2 Detuning and tolerances 53
8.2.1 General 53
8.2.2 Detuning factors 54
8.2.3 Resistance variations 55
8.2.4 Modelling 55
8.3 Network impedance for performance calculations 55
8.3.1 General 55
8.3.2 Network modelling using impedance envelopes 56
8.3.3 Sector diagram 57
8.3.4 Circle diagram 58
8.3.5 Discrete polygons 59
8.3.6 Zero-sequence impedance modelling 61
8.3.7 Detailed modelling of AC network for performance calculation 61
8.4 Outages of filter banks and sub-banks 62
8.5 Considerations of probability 63
8.6 Flexibility regarding compliance 65
8.7 Ratings of the harmonic filter equipment 65
9 Filter switching and reactive power management 66

9.1 General 66
9.2 Reactive power interchange with AC network 66
9.2.1 General 66
9.2.2 Impact on reactive compensation and filter equipment 66
9.2.3 Evaluation of reactive power interchange 67
9.3 HVDC converter reactive power capability 68
9.4 Bank/sub-bank definitions and sizing 68
9.4.1 General 68
9.4.2 Sizing 69
9.5 Hysteresis in switching points 71
9.6 Converter Q-V control near switching points 72
9.7 Operation at increased converter control angles 72
9.8 Filter switching sequence and harmonic performance 72
9.9 Demarcation of responsibilities 73
9.9.1 General 73
9.9.2 Customer 73
9.9.3 Contractor 74
10 Customer specified parameters and requirements 74
10.1 General 74
10.2 AC system parameters 74
10.2.1 Voltage 74
10.2.2 Voltage unbalance 75
10.2.3 Frequency 75
10.2.4 Short circuit level 75
10.2.5 Filter switching 75
10.2.6 Reactive power interchange 76
10.2.7 System harmonic impedance 76
10.2.8 Zero sequence data 76
10.2.9 System earthing 76
10.2.10 Insulation level 76
10.2.11 Creepage distances 76
10.2.12 Pre-existing voltage distortion 76
10.3 Harmonic distortion requirements 77
10.3.1 General 77
10.3.2 Redundancy requirements 77
10.4 Environmental conditions 77
10.4.1 Temperature 77
10.4.2 Pollution 77
10.4.3 Wind 77
10.4.4 Ice and snow loading (if applicable) 78
10.4.5 Solar radiation 78
10.4.6 Isokeraunic levels 78
10.4.7 Seismic requirements 78
10.4.8 Audible noise 78
10.5 Electrical environment 78
10.6 Requirements for filter arrangements and components 79
10.6.1 Filter arrangements 79
10.6.2 Filter capacitors 79
10.6.3 Test requirements 79

10.7 Protection of filters 79
10.8 Loss evaluation 79
10.9 Field measurements and verifications 79
10.10 General requirements 79
11 Future developments 80
11.1 General 80
11.2 Non-standard filter technology 80
11.2.1 General 80
11.2.2 Automatically tuned reactors 80
11.2.3 Single-phase redundancy 83
11.2.4 Stand-along active filters 84
11.2.5 Compact design 86
11.3 Other LCC converter technology 86
11.3.1 General 86
11.3.2 Series commutated converters 86
11.3.3 Transformerless converters 89
11.3.4 Unit connection 89
11.4 Changing external environment 90
11.4.1 Increased pre-existing levels of harmonic distortion 90
11.4.2 Developments in communication technology 90
11.4.3 Changes in structure of the power supply industry 91
11.4.4 Focus on power quality 91
11.4.5 Fewer large synchronous generators and more renewable and distributed generation 91
Annex A (informative) Alternative type of procurement procedure 92
Annex B (informative) Formulae for calculating the characteristic harmonics of a bridge converter 93
Annex C (informative) Definition of telephone interference parameters 95
C.1 General 95
C.2 Criteria according to European practice 95
C.3 Criteria according to North American practice 96
C.4 Discussion 98
Annex D (informative) Equivalent frequency deviation 99
Annex E (informative) Reactive power management 100
E.1 HVDC converter reactive power capability 100
E.1.1 Steady-state capability 100
E.1.2 Temporary capability 102
E.2 Converter Q-V control near switching points 103
E.3 Step change in voltage on switching a filter 104
Bibliography 106

Figure 1 – Idealized current waveforms on the AC side of converter transformer 29
Figure 2 – Realistic current waveforms on the AC side of converter transformer including effect of non-idealities 30
Figure 3 – Comparison of harmonic content of current waveform under idealized and realistic conditions 31
Figure 4 – Typical variation of characteristic harmonic magnitude with direct current 34
Figure 5 – Single tuned filter and frequency response 41

Figure 6 – Double tuned filter and frequency response 42
Figure 7 – Triple tuned filter and frequency response 44
Figure 8 – 2nd order damped filter and frequency response 46
Figure 9 – 3rd order damped filter and frequency response 46
Figure 10 – C-type filter and frequency response 47
Figure 11 – Double tuned damped filter and frequency response 48
Figure 12 – Circuit model for filter calculations 51
Figure 13 – AC system impedance general sector diagram, with minimum impedance 58
Figure 14 – AC system impedance general sector diagram, with minimum resistance 58
Figure 15 – AC system impedance general circle diagram, with minimum resistance 59
Figure 16 – Example of harmonic impedances for harmonics of order 2 to 4 60
Figure 17 – Example of harmonic impedances for harmonics of order 5 to 8 60
Figure 18 – Example of harmonic impedances for harmonics of order 9 to 13 61
Figure 19 – Example of harmonic impedances for harmonics of order 14 to 49 61
Figure 20 – Illustration of basic voltage quality concepts with time/location statistics covering the whole system (adapted from IEC TR 61000-3-6:2008) 64
Figure 21 – Example of range of operation where specifications on harmonic levels are not met for a filter scheme solution 65
Figure 22 – Branch, sub-bank and bank definition 69
Figure 23 – Typical switching sequence 73
Figure 24 – Reactive power components 74
Figure 25 – Design principle of a self-tuned reactor using DC control current in an orthogonal winding 82
Figure 26 – Control principle for self-tuned filter 82
Figure 27 – One method of switching a redundant single phase filter 84
Figure 28 – Various possible configurations of series compensated HVDC converters 88
Figure E.1 – Capability diagram of a converter under different control strategies 100
Figure E.2 – Converter capability with γ_{min} = 17°, γ_{max} = 40°, α_{min} = 5°, α_{max} = 35° and U_{diomax} = 1,2U_{dioN} 101
Figure E.3 – Reactive power absorption of a rectifier as a function of α with U_{dio} = U_{dioN}, d_x = 9,4 % and d_r = 0,2 % 103
Figure E.4 – Reactive power absorption of a inverter as a function of γ with U_{dio} = U_{dioN}, d_x = 9,4 % and d_r = 0,2 % 103

INTERNATIONAL ELECTROTECHNICAL COMMISSION

_____

HIGH-VOLTAGE DIRECT CURRENT (HVDC) SYSTEMS – GUIDANCE TO THE SPECIFICATION AND DESIGN EVALUATION OF AC FILTERS –

Part 1: Overview

FOREWORD

1) The International Electrotechnical Commission (IEC) is a worldwide organization for standardization comprising all national electrotechnical committees (IEC National Committees). The object of IEC is to promote international co-operation on all questions concerning standardization in the electrical and electronic fields. To this end and in addition to other activities, IEC publishes International Standards, Technical Specifications, Technical Reports, Publicly Available Specifications (PAS) and Guides (hereafter referred to as "IEC Publication(s)"). Their preparation is entrusted to technical committees; any IEC National Committee interested in the subject dealt with may participate in this preparatory work. International, governmental and non-governmental organizations liaising with the IEC also participate in this preparation. IEC collaborates closely with the International Organization for Standardization (ISO) in accordance with conditions determined by agreement between the two organizations.
2) The formal decisions or agreements of IEC on technical matters express, as nearly as possible, an international consensus of opinion on the relevant subjects since each technical committee has representation from all interested IEC National Committees.
3) IEC Publications have the form of recommendations for international use and are accepted by IEC National Committees in that sense. While all reasonable efforts are made to ensure that the technical content of IEC Publications is accurate, IEC cannot be held responsible for the way in which they are used or for any misinterpretation by any end user.
4) In order to promote international uniformity, IEC National Committees undertake to apply IEC Publications transparently to the maximum extent possible in their national and regional publications. Any divergence between any IEC Publication and the corresponding national or regional publication shall be clearly indicated in the latter.
5) IEC itself does not provide any attestation of conformity. Independent certification bodies provide conformity assessment services and, in some areas, access to IEC marks of conformity. IEC is not responsible for any services carried out by independent certification bodies.
6) All users should ensure that they have the latest edition of this publication.
7) No liability shall attach to IEC or its directors, employees, servants or agents including individual experts and members of its technical committees and IEC National Committees for any personal injury, property damage or other damage of any nature whatsoever, whether direct or indirect, or for costs (including legal fees) and expenses arising out of the publication, use of, or reliance upon, this IEC Publication or any other IEC Publications.
8) Attention is drawn to the Normative references cited in this publication. Use of the referenced publications is indispensable for the correct application of this publication.
9) Attention is drawn to the possibility that some of the elements of this IEC Publication may be the subject of patent rights. IEC shall not be held responsible for identifying any or all such patent rights.

IEC TR 62001-1 has been prepared by subcommittee 22F: Power electronics for electrical transmission and distribution systems, of IEC technical committee 22: Power electronic systems and equipment. It is a Technical Report.

This second edition cancels and replaces the first edition published in 2016. This edition constitutes a technical revision.

This edition includes the following significant technical changes with respect to the previous edition:

a) general updating of the document to reflect changes in practice;
b) 10.2.4 on fuseless capacitors has been transferred to IEC TR 62001-4;
c) Clause 11 on future developments has been expanded;
d) 10.3.3 and Annex F on voltage sourced converters have been deleted as their content is covered by IEC TR 62543.

The text of this Technical Report is based on the following documents:

DTR	Report on voting
22F/614/DTR	22F/623A/RVDTR

Full information on the voting for its approval can be found in the report on voting indicated in the above table.

The language used for the development of this Technical Report is English.

This document was drafted in accordance with ISO/IEC Directives, Part 2, and developed in accordance with ISO/IEC Directives, Part 1 and ISO/IEC Directives, IEC Supplement, available at www.iec.ch/members_experts/refdocs. The main document types developed by IEC are described in greater detail at www.iec.ch/standardsdev/publications.

A list of all parts in the IEC TR 62001 series, published under the general title *High-voltage direct current (HVDC) systems – Guidance to the specification and design evaluation of AC filters*, can be found on the IEC website.

The committee has decided that the contents of this document will remain unchanged until the stability date indicated on the IEC website under webstore.iec.ch in the data related to the specific document. At this date, the document will be

- reconfirmed,
- withdrawn,
- replaced by a revised edition, or
- amended.

IMPORTANT – The "colour inside" logo on the cover page of this document indicates that it contains colours which are considered to be useful for the correct understanding of its contents. Users should therefore print this document using a colour printer.

INTRODUCTION

The IEC TR 62001 series is structured in five parts:

IEC TR 62001-1 – Overview

This part concerns specifications of AC filters for high-voltage direct current (HVDC) systems with line-commutated converters, permissible distortion limits, harmonic generation, filter arrangements, filter performance calculation, filter switching and reactive power management and customer specified parameters and requirements.

IEC TR 62001-2 – Performance

This part deals with current-based interference criteria, field measurements and verification.

IEC TR 62001-3 – Modelling

This part addresses the harmonic interaction across converters, pre-existing harmonics, AC network impedance modelling, simulation of AC filter performance.

IEC TR 62001-4 – Equipment

This part concerns steady-state and transient ratings of AC filters and their components, power losses, audible noise, design issues and special applications, filter protection, seismic requirements, equipment design and test parameters.

IEC TR 62001-5[1] – AC side harmonics and appropriate harmonic limits for high-voltage direct current (HVDC) systems with voltage sourced converters (VSC)

This document concerns specific issues of AC filter design related to VSC HVDC systems.

Parts 1 to 4 are written with focus on line commutated converters.

[1] Under preparation. Stage at the time of publication: IEC/RPUB 62001-5:2021.

HIGH-VOLTAGE DIRECT CURRENT (HVDC) SYSTEMS – GUIDANCE TO THE SPECIFICATION AND DESIGN EVALUATION OF AC FILTERS –

Part 1: Overview

1 Scope

This part of IEC 62001, which is a Technical Report, deals with the specification and design evaluation of AC side harmonic performance and AC side filters for HVDC schemes. It is intended to be primarily for the use of the utilities and consultants who are responsible for issuing the specifications for new HVDC projects and evaluating designs proposed by prospective suppliers.

This document provides guidance on the specifications of AC filters for high-voltage direct current (HVDC) systems with line-commutated converters and filter performance calculation.

The scope of this document covers AC side filtering for the frequency range of interest in terms of harmonic distortion and audible frequency disturbances. Where the term "HVDC converter" or "HVDC station" is referred to without qualification, in this document, it is understood to refer to LCC technology. It excludes filters designed to be effective in the power line carrier (PLC) and radio interference spectra.

The bulk of this document concentrates on the "conventional" AC filter technology and LCC (line-commutated converter) HVDC. Voltage sourced converter (VSC) specific issues are discussed in CIGRE Technical Brochure 754 [1][2] and in IEC TR 62001-5 [2].

2 Normative references

There are no normative references in this document.

---

2 Numbers in square brackets refer to the Bibliography.